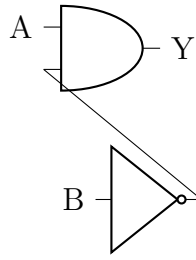


Consider the logic circuit below:



Complete the truth table for inputs A and B, and output Y.